

UIL Circuits


Key

P12. Jack has a circuit with three resistors connected in series. Their respective resistances are  $6.00\ \Omega$ ,  $9.00\ \Omega$  and  $15.0\ \Omega$ . If he connects this arrangement to a  $12.0\text{-V}$  battery, what is the voltage drop across the  $9.00\text{-}\Omega$  resistor?

- A)  $7.20\ \text{V}$
- B)  $6.00\ \text{V}$
- C)  $4.80\ \text{V}$
- D)  $3.60\ \text{V}$**
- E)  $2.40\ \text{V}$

$V = IR$

$R_T = 30$   
 $V_T = 12$   
 $I_T = .4$

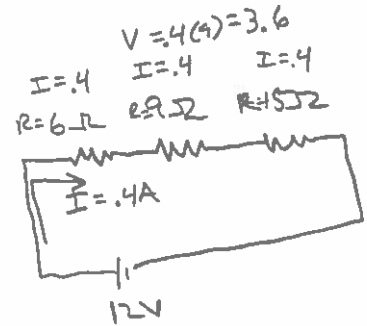


P12. Eric has a circuit with four resistors connected in parallel. Their respective resistances are  $6.00\ \Omega$ ,  $9.00\ \Omega$ ,  $12.0\ \Omega$  and  $15.0\ \Omega$ . If he connects this arrangement to a  $24.0\text{-V}$  battery, what is the current that flows through the  $12.0\text{-}\Omega$  resistor?

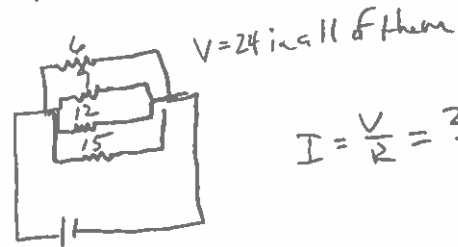- A)  $1.52\ \text{A}$
- B)  $1.64\ \text{A}$
- C)  $1.76\ \text{A}$
- D)  $1.88\ \text{A}$
- E)  $2.00\ \text{A}$**

$V = IR$


$R_T = \left(\frac{1}{6} + \frac{1}{9} + \frac{1}{12} + \frac{1}{15}\right)^{-1} = 2.34\ \Omega$   
 $V_T = 24\ \text{V}$   
 $I_T = 10.27\ \text{A}$



$I = \frac{V}{R} = \frac{24}{12} = 2\ \text{A}$

P12. Joe has three resistors that have respective resistances of  $18.0\ \Omega$ ,  $24.0\ \Omega$  and  $36.0\ \Omega$ . He connects them in series and then connects this arrangement to a  $12.0\text{-V}$  battery. Find the voltage drop across the  $24\text{-}\Omega$  resistor.

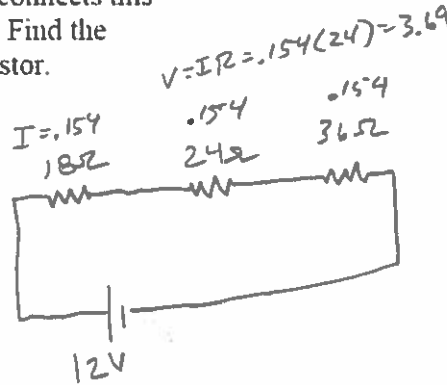
- A)  $2.77\ \text{V}$
- B)  $3.23\ \text{V}$
- C)  $3.69\ \text{V}$**
- D)  $4.57\ \text{V}$
- E)  $5.44\ \text{V}$



$R_T = 78\ \Omega$   
 $V_T = 12\ \text{V}$   
 $I_T = .154\ \text{A}$


UIL Circuits

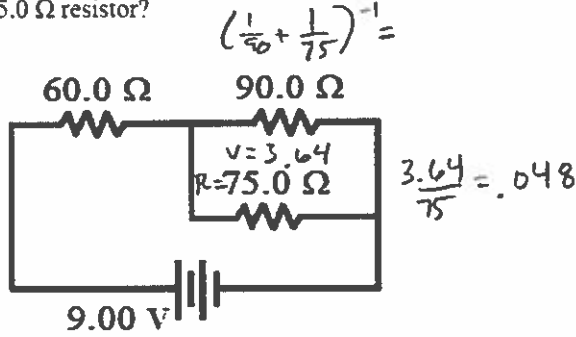P07. Given the circuit shown, what is the current flowing in the 75.0 Ω resistor?




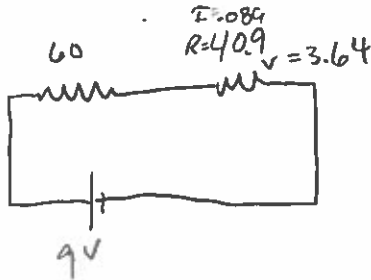- A) 120 mA
- B) 89.2 mA
- C) 48.6 mA
- D) 40.5 mA
- E) 19.8 mA

$R_T = 100.9$   
 $V_T = 9V$   
 $I_T = .089$



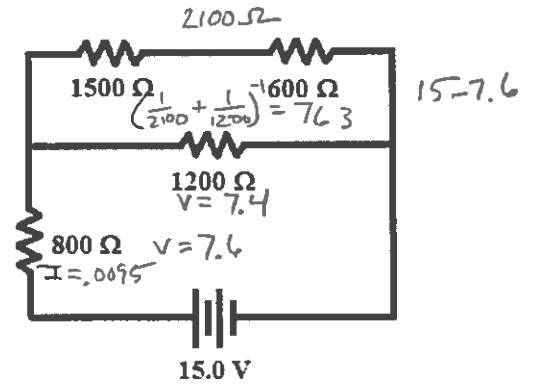P07. Given the circuit shown, determine the current flowing through the 1200Ω resistor.




- A) 6.10 mA
- B) 7.50 mA
- C) 9.59 mA
- D) 10.1 mA
- E) 12.5 mA

$R_T = 1563 \Omega$   
 $V_T = 15V$   
 $I_T = .0095A$

$V = IR$   
 $7.4 = I(1200)$   
 $I = .0061$

UIL Circuits

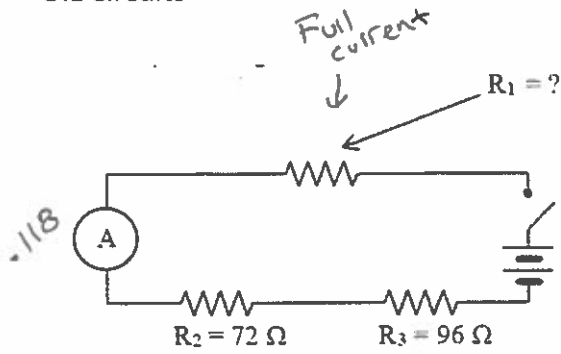

$$R_T = 168 + R_1$$

$$V_T = 24 \text{ V}$$

$$I_T = 0.118 \text{ A}$$

$$V = I R_T$$

$$24 = 0.118(168 + R_1)$$


$$R_1 = 35.4$$

P12. Christina has a circuit with a 24.0-V battery, a switch, three resistors, and an ammeter. When the switch is closed, the ammeter reads 0.118 A. What is the resistance of the top resistor?

- A) 35.4 Ω
- B) 37.6 Ω
- C) 39.8 Ω
- D) 42.0 Ω
- E) 44.2 Ω


P08. Given the following circuit, what is the current flowing in the 150.0 Ω resistor?

hard

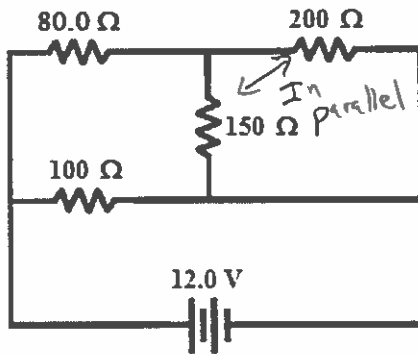

think like this

$$I = 1.92 / 12 = 0.16$$

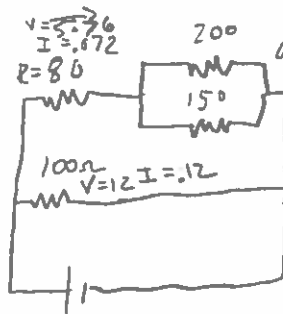

$$R_T = \left( \frac{1}{165.71} + \frac{1}{100} \right)^{-1} = 62.36 \Omega$$

$$V_T = 12 \text{ V}$$

$$I_T = 0.192 \text{ A}$$

- A) 23.4 mA
- B) 30.4 mA
- C) 41.4 mA
- D) 52.7 mA
- E) 72.4 mA


P12. Joe has three capacitors that have respective capacitances of 246 nF, 432 nF and 678 nF. If he connects them in series, what will the net capacitance be?

- A) 1360 nF
- B) 1050 nF
- C) 741 nF
- D) 434 nF
- E) 127 nF

$$\left( \frac{1}{246} + \frac{1}{432} + \frac{1}{678} \right)^{-1} = 127$$

UIL Circuits

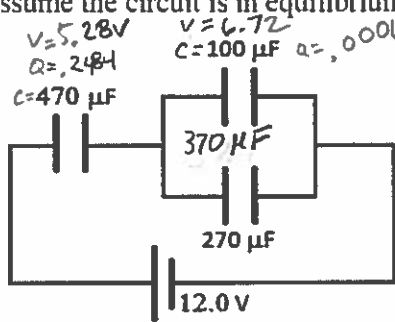P08. Given the capacitor circuit shown, what is the charge stored on the  $100\mu\text{F}$  capacitor? You may assume the circuit is in equilibrium.



$V = 5.28\text{V}$   
 $Q = 2484$   
 $C = 470\ \mu\text{F}$

$V = 6.72$   
 $C = 100\ \mu\text{F}$   
 $Q = 0.000672$

$$C_T = \left(\frac{1}{470} + \frac{1}{370}\right)^{-1} = 207.624\ \mu\text{F}$$

$$V_T = 12\text{V}$$


$$Q_T = 12(207.624) = 2491.488\ \mu\text{C}$$

- A)  $161\ \mu\text{C}$
- B)  $671\ \mu\text{C}$**
- C)  $1200\ \mu\text{C}$
- D)  $2140\ \mu\text{C}$
- E)  $2720\ \mu\text{C}$

$$C = \frac{Q}{V}$$

$$Q = CV$$

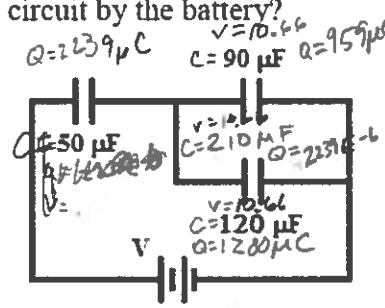P12. If the charge stored on the  $120\mu\text{F}$  capacitor in this circuit is known to be  $1280\mu\text{C}$ , what is the voltage supplied to the circuit by the battery?



$Q = 2239\ \mu\text{C}$   
 $V = 10.66$   
 $C = 90\ \mu\text{F}$   
 $Q = 959\ \mu\text{C}$

$Q = 50\ \mu\text{F}$   
 $V = ?$

$V = 10.66$   
 $C = 210\ \mu\text{F}$   
 $Q = 2239\ \mu\text{C}$

$V = 10.66$   
 $C = 120\ \mu\text{F}$   
 $Q = 1280\ \mu\text{C}$

$$C_T = \left(\frac{1}{50} + \frac{1}{210}\right)^{-1} = 40.38\ \mu\text{F}$$

$$Q_T = 959 + 1280 = 2239\ \mu\text{C}$$

$$V_T = 56\text{V}$$

- A)  $55.5\text{V}$**
- B)  $36.3\text{V}$
- C)  $31.7\text{V}$
- D)  $21.6\text{V}$
- E)  $10.7\text{V}$

$$C = \frac{Q}{V}$$

$$V = \frac{Q}{C}$$

$$Q = CV$$